

CONFIDENTIAL AND PROPRIETARY - AEI SYSTEMS
Copyright AEI Systems © 2006-2024 All Rights Reserved

[illegible]

[illegible]

[illegible]

TPS61028_Avg	TI	Power IC	TPS61028 (in Examples/117P961028)	Adjustable, 1.5A Switch, 96% Efficient Boost Converter with Down-Mode, OPM-10	3.8	tps61028avg	Boost	Frequency Response	96% Efficient Synchronous Boost Converter
TPS61030	TI	Power IC	TPS61030 (in Examples/117P961030/TPS61030_PSPICE_TRANS)	Adjustable, 4.4A Switch, 96% Efficient Boost Converter	3.1	tps61030	Boost	Startup, transient	3.3V input, 6V output, 250mA load
TPS61031	TI	Power IC	TPS61031 (in Examples/117P961031/TPS61031_PSPICE_TRANS)	3.3-V Output, 1-A, 96% Efficient Boost Converter	3.1	tps61031	Boost	Startup, transient	1.8V input, 3.3V output, 100mA load
TPS61032	TI	Power IC	TPS61032 (in Examples/117P961032/TPS61032_PSPICE_TRANS)	5-V Output, 1-A, 96% Efficient Boost Converter	3.1	tps61032	Boost	Startup, transient	2.5V input, 3.3V output, 250mA load
TPS61040	TI	Power IC	TPS61040 (in Examples/117P961040)	Evaluation Module	4.8	SLV9413E	Switch boost converter for LCD and LED applications	Transient	
TPS61041	TI	Power IC	TPS61041 (in Examples/117P961041)	Evaluation Module	4.8	SLV9413E	Switch boost converter for LCD and LED applications	Transient	
TPS61085	TI	Power IC	TPS61085 (in Examples/117P961085/TPS61085_PSPICE_TRANS)	18.5V, 3A, 650kHz / 1.2MHz Step-Up DC-DC Converter	3.1	tps61085	Boost	Startup, transient	6V input, 12V output, 300mA load
TPS61086	TI	Power IC	TPS61086 (in Examples/117P961086/TPS61086_PSPICE_TRANS)	18.5V PFPM PWM High Efficiency Step-Up DC-DC Converter	3.1	tps61086	Boost	Startup, transient	6V input, 12V output, 1mA load
TPS61087	TI	Power IC	TPS61087 (in Examples/117P961087/TPS61087_PSPICE_TRANS)	18.5V, 3.2A, 650kHz / 1.2MHz Step-Up DC-DC Converter	3.1	tps61087	Boost	Startup, transient	2.5V input, 18V output, 500mA load
TPS61170	TI	Power IC	TPS61170 (in Examples/117P961170/TPS61170_PSPICE_TRANS)	18.5V, 3.2A, 650kHz / 1.2MHz Step-Up DC-DC Converter	4.1	tps61087	Boost	Startup, transient	2.5V input, 18V output, 500mA load
TPS62040	TI	Power IC	TPS62040 (in Examples/117P962040)	3MHz 1.8A Step Down Converter	4.8	SLV8A95	Low-voltage step-down converter	Transient	
TPS62045	TI	Power IC	TPS62045 (in Examples/117P962045)	3-MHz 1A Step Down Converter	4.8	SLV1384	Low-voltage step-down converter	Transient	
TPS62067	TI	Power IC	TPS62067 (in Examples/117P962067)	3-MHz 2A Step Down Converter	4.8	SLV833A	high frequency synchronous step down DC-DC converter	Steady-state, transient	
TPS62120	TI	Power IC	TPS62120 (in Examples/117P962120)	10V 75mA High Efficiency Buck Converter	4.8	SLV8AD5	high-efficiency synchronous step down DC-DC converter	Steady-state, transient	
TPS62122	TI	Power IC	TPS62122 (in Examples/117P962122)	10V 75mA High Efficiency Buck Converter	4.8	SLV8AD5	high-efficiency synchronous step down DC-DC converter	Steady-state, transient	
TPS62230	TI	Power IC	TPS62230 (in Examples/117P962230)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS62231	TI	Power IC	TPS62231 (in Examples/117P962231)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS622310	TI	Power IC	TPS622310 (in Examples/117P9622310)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS622311	TI	Power IC	TPS622311 (in Examples/117P9622311)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS622312	TI	Power IC	TPS622312 (in Examples/117P9622312)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS622313	TI	Power IC	TPS622313 (in Examples/117P9622313)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS622314	TI	Power IC	TPS622314 (in Examples/117P9622314)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS622318	TI	Power IC	TPS622318 (in Examples/117P9622318)	3-MHz Ultra-small step down converter	4.1	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS62232	TI	Power IC	TPS62232 (in Examples/117P962232)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS62233	TI	Power IC	TPS62233 (in Examples/117P962233)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	
TPS62234	TI	Power IC	TPS62234 (in Examples/117P962234)	3-MHz Ultra-small step down converter	4.8a	SLVU312	high frequency synchronous step down DC-DC converter	Transient	